


## EE304 Microelectronics Homework 4

Due date: 13:00, 15th, December

Solve problems below.


#1. A CMOS NAND gate drives a load capacitance of 20fF. Suppose the input waveforms are as shown below, each having a frequency of  $f_1 = 500$  MHz. Draw the output waveform and calculate the power dissipated by the gate. Neglect the crowbar current.

[20 Points]

 


#2. For NMOS shown below, draw the dual PMOS section, construct the overall CMOS gate, and determine the logical function performed by the gate.

[20 Points]

 


#3. For below figure, if  $V_1 = 0.8V$ ,  $V_2 = 1.1$  and  $V_3 = 0.5V$ .  $R_1 = R_2 = R_3 = 5k\Omega$  and  $R_F = 10k\Omega$   
 $A_0 = \infty$ , find  $V_{out}$ . The notation at the positive terminal of the operational amplifier is the  
 symbol for ground or  $0V$ .

[20 Points]

 


#4. For the circuit shown below, CS stage with degeneration (MOS connected load), find  
 $R_{out}$  using equivalent circuit.

[20 Points]

 


#5. Sketch  $I_X$  as a function of  $V_X$  for the circuits (a) and (b) shown below. Assume  $V_X$  goes from 0 to  $V_{DD} = 1.8V$  and  $V_{TH} = 0.4V$ . Also,  $\lambda = 0$ . Determine at what value of the device changes its region of operation. Specify operating regions on your I-V graph.

[20 Points]

 

(a)

 

(b)

#### NOTE

- If you drive answer without sufficient explanation, your score will not be given fully.

- There is final exam 15<sup>th</sup>, December. Therefore, you should submit your homework4 just before the final exam begins. Of course, submitting late is NOT acceptable.

- You should write all your answers in English.